# HAND OUT ON TUNED VOLTAGE AMPLIFIER

## **A- TUNED VOLTAGE AMPLIFIER**

An amplifier used to amplify a selected frequency or a narrow band of frequencies, is known as Tuned voltage Amplifier.

A Here load circuit is a tank circuit so that it can be tuned to pass or amplify selection of a desired frequency or a narrow band of frequencies.

The phenomena of resonance as occurs in the tank circuit which is capable of selecting a particular or relative narrow band of frequencies, is used in such amplifier.

⇒ The resonant frequency of the tuned circuit is centre of selected frequency band .

Basic Circuit of a tuned voltage amplifier is shown below:-



There are two main types of tuned amplifiers.

- 1- Single tuned amplifier
- 2- Double tuned amplifier

1- Single Tuned Amplifier- An amplified with a single tuner section being at the collector of the amplifier circuit is called as Single tune amplifier circuit.

2-Double tuned amplifier- W o tuner circuits are used at collector of amplifier circuit, then such an amplifier is known as double toned amplifier.

## **B-Resonance Circuits :**

⇒ The phenomenon of resonance occurs only in ac circuits containing an inductance L and capacitance C with two element connected in series and parallel. The Circuit also contains resistance R which may the effective resistance of the coil L itself or a resistance deliberately introduced in the circuit for certain reason.

⇒When such a circuit is connected across an ac supply, in normal condition, the above parameters may behave as an inductive circuit or a capacitive circuit. However when at a particular supply frequency the inductive reactance becomes equal to capacitive reactance, the circuit then behaves as purely resistive circuit.

⇒In such situation, current supplied to the circuit is in phase with supply voltage & this phenomenon is called resonance and the corresponding frequency as resonant frequency.

# B-1-Series resonant circuit and its bandwidth

⇒ In a series resonant circuit, an inductor and a capacitor is connected in series across an ac source as shown in the diagram:



 $\Rightarrow$  At any frequency f of supply voltage, inductive reactance is given as XL =  $2\pi$  f L Capacitive reactance  $Xc = 1/2\pi fC$ Whereas total impedance of the circuit is given as  $Zs = - \left[ R^2 + (x_1 - x_e)^2 \right]$ 



⇒As we see that both inductive & capacitive reactance (XL & Xc) dependent supply frequency f. XL is directly proportional to frequency f whereas Xc is inversely proportional to supply frequency f. ⇒ The variation of XL & Xc with respect to supply frequency is shown the below graph:



⇒As we see in the graph, at particular frequency f, both XL & Xc are equal & at that point both curves intersect each other. The frequency at which XL = Xc, is known as resonant frequency & value of fr is calculated as :

$$f_r = 1/2\pi VLC$$

# **B-2-Characteristics of Series resonant circuit**

1-Impedance of series resonant circuit is minimum at resonant frequency & its value increases when frequency decreases or increases than the resonant frequency.

2- The magnitude of current flowing through series resonant circuit is inversely proportional to resistance of the series resonant circuit.

3- the Q value of series resonant circuit varies inversely with the circuit resistance where Q is known as quality factor of the circuit & defined as the ratio of voltage drop across L or C to the voltage drop across R at series resonance. This quality factor is a figure of merit.

## B-3- Bandwidth of series resonant circuit

⇒ The range of frequency over which circuit current is equal to more than 70.7% of maximum circuit current at resonance is known as bandwidth of series resonant circuit.

 $\Rightarrow$  Typical series resonance circuit is shown adjacently. As shown, circuit current is equal to or greater than 70.7% of maximum current (I= V/R) between frequency range f<sub>1</sub> & f<sub>2</sub>

Therefore Bandwidth BW= f2 - f1

⇒ BW represents the frequency range at which the circuit offers low impedance path.



As we know that steepness of the resonance curve is determined by Q value of the circuit, therefore bandwidth of series resonant circuit may also be decided in terms of resonant frequency & Q value by the following relation:

$$BW = f_2 - f_1 = f_r / Q$$

⇒ It shows that higher the value of Q, smaller the value of bandwidth of a section resonant circuit.

## C-1-Parallel resonant circuit and its bandwidth

⇒ In a parallel resonant circuit, an inductor and a capacitor is connected in parallel across an ac source as shown in the diagram:



⇒Frequency of supply voltage can be varied and at any stage if this frequency is equal to natural or resonance frequency of LC circuit, then resonance will occur.

⇒In such condition, the impedance of tuned circuit becomes maximum & the circuit draws a minimum current from the source.

 $\Rightarrow$  Assume that current drawn by inductor is IL & that by capacitor is IC & IL lags behind the voltage by some angle say  $\phi_L$ . At resonance the resultant current I drawn by the circuit must be in phase with the applied voltage.

 $\Rightarrow$  If f<sub>r</sub> is resonance frequency then in LC parallel tuned circuit, the condition of resonance is obtained when : Ic = IL Sin  $\phi$ L

Where  $I_L = V/Z_L$ ,  $Sin \phi_L = X_L/Z_L and I_C = V/X_C$ Therefore,  $V/X_C = V/Z_L \times X_L/Z_L$ Or  $Z_L^2 = X_L \cdot X_C$ Or  $(R^2 + X_L^2) = X_L \cdot X_C$ Or  $R^2 + (2\pi f_r L)^2 = 2\pi f_r L/2\pi f_r C = L/C$ 

Or 
$$(2\pi f_r L)^2 = L/C - R^2$$

⇒ Usually value of R being very small, can be neglected & then Resonant frequency for a parallel tuned circuit is given as :

$$f_r = 1/2\pi VLC$$

Ch 5 4.1 Electronic Circuit

## C-2-Characteristics of Parallel resonant circuit

1-Impedance of parallel resonant circuit is maximum at resonant frequency & its value decreases rapidly when frequency is changed above or below the resonant frequency. This quality makes parallel resonant circuit good for selecting desired frequency & rejecting unwanted frequency.

2- The magnitude of current flowing through parallel resonant circuit is very small at resonant frequency & its value changes rapidly when frequency is changed above or below resonant frequency.

3- The most important characteristic of a parallel resonant circuit is its property of selectivity, which in turn depends on the sharpness of resonance curve. Sharpness is decided by Q factor which varies inversely with the circuit resistance. Here Q is defined as the ratio of inductive reactance of coil at resonance to its resistance.

## C-3- Bandwidth of Parallel resonant circuit

 $\Rightarrow$  The bandwidth of a parallel resonance circuit is defined in exactly the same way as for the series resonance circuit and is given as BW= f<sub>2</sub> - f<sub>1</sub>

 $\Rightarrow$  Where  $f_2$  is upper and  $f_1$  is lower cut-off frequencies & are equal to 70.7% of its maximum resonant value.  $(0.707 \times 1)^2$  R as shown in the diagram :



 $\Rightarrow$  As with the series circuit, if the resonant frequency remains constant, an increase in the quality factor, **Q** will cause a decrease in the bandwidth and likewise, a decrease in the quality factor will cause an increase in the bandwidth as defined **b**:

$$BW = f_r / Q \text{ or } BW = f_2 - f_1$$

 $\Rightarrow$  Also changing the ratio between the inductor, L and the capacitor, C, or the value of the resistance, R the bandwidth and therefore the frequency response of the circuit will be changed for a fixed resonant frequency.

⇒ This technique is used extensively in tuning circuits for radio and television transmitters and receivers.

# D-Single Tuned Amplifier and its frequency response characteristics

⇒ Single Tuned Amplifier is shown below where a parallel resonant circuit is connected in the collector :



⇒ Usually the capacitor used in resonant circuit is variable & value of L & C is chosen in such a way that resonant frequency is equal to frequency of signal to be amplified.

⇒ The biasing network used is designed for class-C operation. The output of the amplifier may be obtained in either of two ways:

1- By a coupling capacitor

2- By a secondary coil magnetically coupled to inductive coil of the resonant circuit.

⇒ The voltage gain of a single tuned amplifier is given by the following Expression:

#### $A = \beta Z_r/r_i$

where  $\beta$  = Current amplification factor of transistor

Z<sub>r</sub> = Impedance of the resonant circuit at resonant frequency

#### r<sub>i</sub>= Input resistance of the transistor

⇒ The voltage gain of this amplifier is very high since impedance of parallel resonant circuit at resonant frequency.

⇒ FREQUENCY RESPONSE : The graph drawn between voltage gain & frequency is known as frequency response curve . The frequency response curve of single tuned amplifier is shown below:



As the impedance of the resonant circuit is maximum at resonant frequency, the voltage gain will also be maximum at this frequency.

⇒ The voltage gain decreases when frequency varies on either side of the resonant frequency.

⇒ The range of frequency over which an of the amplifier is equal to more than 70.7% of maximum value of voltage gain is known as bandwidth & is given as

 $BW = f_r/Q$ 

A high Q- factor circuit give a high Av but at the same time , it will give much reduced band with because bandwidth is inversely proportional to the Q- factor .

## ADVANTAGE OF SINGLE TUNED AMPLIFIER:

- 1- Less power loss due to the lack of collector resistance.
- 2- High Selectivity.

#### DISADVANTAGE OF SINGLE TUNED AMPLIFIER:

Gain bandwidth product is small

#### APPLICATIONS OF SINGLE TUNED AMPLIFIER

1-This amplifier is used in the primary internal stage of the radio receiver wherever the selection of the front end can be done using an RF amplifier.

2- This amplifier can be used in television circuits.

# E- Double tuned voltage amplifier and its frequency response characteristics

 $\Rightarrow$  The circuit arrangement of double tuned voltage amplifier is same as single tuned voltage amplifier except the difference that now instead of one tuned circuit, two tuned circuits - one L<sub>1</sub>-C<sub>1</sub> in the collector & other L<sub>2</sub> -C<sub>2</sub> in the output are used as shown in the below diagram:



⇒ A change in the coupling of the two tuned circuits results in change in the shape of the Frequency response curve.

⇒ By proper adjustment of the coupling between the two coils of the two tuned circuits, the required results(High selectivity, high Voltage gain and required bandwidth) may be obtained.

⇒ FREQUENCY RESPONSE : The graph drawn between voltage gain & frequency is known as frequency response curve . The frequency response curve of single tuned amplifier is shown below:



 $\Rightarrow$  The frequency response of a double tuned amplifier depends upon degree of magnetic coupling or coefficient of coupling between the two coils L<sub>1</sub> & L<sub>2</sub> . In fact, the load resistance is transferred to collector through this coupling & it affects frequency response curve.

 $\Rightarrow$  In case the two coils are parced separately, the primary coil's (L<sub>1</sub>) flux linkages will not link to the secondary coil (L<sub>2</sub>). At this state, these coils have loose coupling. The reflected resistance from the L2 coil on this state is minute & the resonance curve is sharp.

 $\Rightarrow$  When the two coils are arranged together, then they have tight coupling. Below these forms, the reflected resistance will be huge & the curve is lesser.

 $\Rightarrow$  The bandwidth of this amplifier is shown in the above figure which states that the BW rises by the amount of coupling. In a double-tuned circuit, the determining factor is not Q, rather it is coupling. & also when for certain frequency, the coupling is tighter, the bandwidth will be greater

#### Advantages of Double Tuned Amplifier

- 1- Narrow bandwidth.
- 2- Increased Sensitivity with gain

3- Improved Selectivity

#### **Disadvantages of Double Tuned Amplifier**

1- Not suitable for amplification of audio frequencies

2- Due to use of elements like capacitor & inductor, the circuit is costly & bulky.

#### **Applications of Double-tuned Amplifier**

1- In super heterodyne receiver & satellite transponder as an IF (intermediate frequency) amplifier.

2- Used within UHF radio relay systems.

3- Used as extremely narrow-band intermediate frequency amplifier in a spectrum analyzer.